

Analogy Electronics - Regan Dangel

Assignment - 1.1

$$1. \quad V_1 = ?, \quad V_2 = ?$$

$$V_1 = 4i^{\circ}, \quad V_2 = -2i^{\circ}$$

Then,

KVL clockwise from bottom left

$$-32 + Vi - (-8) - V_2 = 0$$

$$-32 + 4i^{\circ} + 8 - (-2i) = 0$$

$$6i^{\circ} = 24$$

$$i^{\circ} = 4A$$

$$V_1 = 4i^{\circ} = 4 \times 4 = 16V$$

$$V_2 = -2(4) = -8V //$$

2. Find V_x and V_o

$$V_x = 10i^o$$

$$V_o = -5i^o$$

KVL clockwise

$$-70 + V_x + 2V_x - V_o = 0$$

$$-70 + 10i^o + 2(10i^o) - (-5i^o) = 0$$

$$-70 + 10i^o + 20i^o + 5i^o = 0$$

$$35i^o = 70$$

$$i = 2A$$

$$V_x = 10(2) = 20V$$

$$V_o = -5(2) = -10V$$

3. Equivalent Resistance (R_{eq})

Right branch: $R_{s1} = 8 + 10 + 6 = 24 \Omega$

First parallel block = 24Ω is parallel to 12Ω

$$R_{p1} = \frac{24 \times 12}{24 + 12} = \frac{288}{36} = 8 \Omega$$

Middle series block: 8Ω is in series with the top 4Ω resistor

$$R_{s2} = 8 + 4 = 12 \Omega$$

Second parallel block: The 12Ω is parallel with 6Ω vertical resistor

$$R_{p2} = \frac{12 \times 6}{12 + 6} = \frac{72}{18} = 4 \Omega$$

Final series block = 4Ω is in series with the input 4Ω and 3Ω Resistor

$$R_{eq} = 4 + 4 + 3 = 11 \Omega$$

4. Equivalent Capacitance (C_{eq})

- Left parallel block : The $50\ \mu\text{F}$ and $70\ \mu\text{F}$ capacitors are in parallel.

$$C_{p1} = 50 + 70 = 120\ \mu\text{F}$$

- Right series block = The $60\ \mu\text{F}$ and $120\ \mu\text{F}$ are series

$$C_{s1} = \frac{60 \times 120}{60 + 120} = \frac{7200}{180} = 40\ \mu\text{F}$$

- Middle parallel block = $40\ \mu\text{F}$ is parallel with the $20\ \mu\text{F}$ vertical capacitor

$$C_{p2} = 40 + 20 = 60\ \mu\text{F}$$

- Final series block = The first equivalent ($120\ \mu\text{F}$) and the new equivalent ($60\ \mu\text{F}$) are in series

$$C_{eq} = \frac{120 \times 60}{120 + 60} = \frac{7200}{180} = 40\ \mu\text{F}$$

Q. 5. Find the Voltage Across Each Capacitor.

1. Find C_{eq} : $60\mu F$ & $30\mu F$ are in series : $\frac{60 \times 30}{60 + 30}$

- This is in parallel with the $= 20\mu F$
 $20\mu F$ capacitor (V_2) : $20 + 20 = 40\mu F$

- This is in series with the $40\mu F$ capacitor (V_1)
 $= \frac{40 \times 40}{40 + 40} = 20\mu F$

2. Find the total Charge : $Q = C_{eq} \times V = 20 \times 150$
 $= 3000 \mu C$

3. Calculate Voltage :

$$V_1 = Q / C_1 = 3000 / 40 = 75V$$

- The remaining voltage drops across the parallel block : $V_2 = 150 - 75 = 75V$

- The charge on the rightmost branch going right
 $= C_{series} \times V_2 = 20 \times 75 = 1500 \mu C$

$$V_3 = 1500 / 60 = 25V$$

$$V_4 = 1500 / 30 = 50V$$

The Ans - $V_1 = 75V$, $V_2 = 75V$, $V_3 = 25V$
& $V_4 = 50V$

Q.6 - Find the Equivalent Inductance (L_{eq})

1. The far-right $20H$, $12H$ and $10H$ inductors are in series: $20 + 12 + 10 = 42H$

2. This $42H$ is in parallel with the $7H$ inductor. $\frac{(42 \times 7)}{42 + 7} = 6H$

3. This $6H$ is in series with the top-left $4H$ and bottom-left $8H$: $4 + 6 + 8 = 18H$

$$L_{eq} = 18H$$

Q.7 : Calculate ladder Network Equivalent inductance

1. Far right : The top 40 mH and vertical 20 mH are in series : $40 + 20 = 60 \text{ mH}$

2. This 60 mH is in parallel with the 30 mH vertical inductor
$$\frac{60 \times 30}{60 + 30} = 20 \text{ mH}$$

3. Move left : This 20 mH is in series with the top 100 mH
$$100 + 20 = 120 \text{ mH}$$

4. This 120 mH is in parallel with the 40 mH vertical inductor
$$\frac{120 \times 30}{120 + 30} = 30 \text{ mH}$$

5. The left 30 mH is in series with the top 20 mH : $20 + 30 = 50 \text{ mH}$

6. Finally, this 50 mH is in parallel with the first vertical 50 mH inductor at the terminals $L_{eq} = \frac{50 \times 50}{50 + 50} = 25 \text{ mH}$

$L_{eq} = 25 \text{ mH}$.